

“Montreal Doppler I” - by Jacques, VE2EMM

IMPORTANT NOTES ABOUT THIS ARCHIVED REPRESENTATION OF THE ORIGINAL WEB PAGES:

- This document was created from archived web pages, the originals having been created by Jacques, VE2EMM - Certain information, URLs and email addresses shown on this page *MAY* be obsolete.
- The original URL was: <http://www.qsl.net/ve2emm/pic-projects/doppler/mtdop1-e.html>
- Because the original author has obsoleted this project, *please be understanding if support cannot be provided by the original author, VE2EMM.*
- This document was created to provide a record of this device, as the originally-created web page may no longer be in existence. This may be helpful if you still wish to construct this project, or if you have one about which you are trying to find information.
- The pictures and diagrams referenced by some of the embedded links in this document may be found at the end of this document.
- ONLY THE TEXT of the user's comments were found in the archive and NOT the pictures. *(Note that the W1EMT and IK4CIE comments consisted only of pictures and are not included – sorry.)*

The Montreal Doppler

FEATURES :

- PIC16C72 controlled
- 32 LEDs display
- Reduced component count, only 4 ICs
- On demand, the antenna switching can be made to +5 volt or to 0 volt
- It will drive the KA4IIA Antenna Switcher, K0OV new wide band Antenna Switcher or the original ROANOKE switcher with resistors added.
- Fine filtering. Bandpass is less than 2Hz
- The display is automatically slow flash to the last good LED when the radio receiver goes squelched
- Overload indication by the processor, the 180 degree lamp fast flash on overload. Modulation does not blink the lamp
- Rock solid software, and it works fine...
- Antenna plan at <http://members.aol.com/homingin/newdopant.html> on the Homingin web site

This version uses the ROANOKE digital filter, a MAX294CPA as a very sharp low pass and a band pass filter. Buy the MAX 294CPA or the MAX293CPA and the MAX 494CPD directly from the Maxim web site.

All the digital functions are taken care by the PIC, it also does some averaging of the returned signal.

Users comments and suggestions.

From Ian, G8PWE

From Mike, K5ATM

From Jay, W1EMT Pictures

From Victor ik4cie Picture

Download the source program and the Hex file here for ham operators only .

Instruction text for the construction and operation of VE2EMM 32 LED DOPPLER.

Schematic diagram V3.07.

Parts list.

A note from MAXIM tech support about the MAX294. My experience with the MAX294 indicates that about 1 in 10 is defective.


Component location

Components location and PCB

PCB in gif format 2X

PRINTED CIRCUIT board drawing in PROTEL EASYTRAX for DOS format.

 A set of PCBs is available from FAR CIRCUITS.



Fine print:

All material on this page is distributed on a WYSIWYG basis and as such I can't take any responsibility for the use of this design and its results. However in saying this it must also be mentioned that every effort has been taken to ensure that it as error free as possible.

[BACK TO HOME PAGE INDEX](#)

Many thanks to Al Waller K3TKJ for graciously hosting my web pages on QSL.NET.

July 16th, 1999

Documentation for VE2EMM 32 LED MONTREAL DOPPLER

1- OPERATING INSTRUCTIONS

While receiving an unmodulated signal, turn up the volume until the 180 degree lamp flashes, then reduce the volume until the 180 degree lamp goes off. The volume is now set. The display will then indicate the direction of the fox.

When the radio receiver goes squelched, the display will slow flash the LED of the last good direction indication.

Calibrate the direction to a known fox by turning the CAL pot, then pressing the reset button will load the new calibration and change the displayed direction.

2- CIRCUIT DESCRIPTION

The signal from the RX goes through a HighPass filter composed of a .01uF cap and a 51k~ resistor, the 10R pot can be replaced by a 10R fixed resistor and the internal speaker can be connected across it through a switch. The signal is then amplified 20 times by the free amp of the MAX294. Output pin 3 from the free amp of the MAX294 goes to amp "A" of the MAX494 rail to rail amplifiers, configured as a 500 Hz bandpass filter. The 1500~ resistor below the BandPass can be adjusted to change the BP frequency. The signal from pin 1 of the MAX494 goes to the input of the MAX294 filter, its knee frequency is determined by the capacitors on pin 1.

The output of the MAX294 goes through a 1M0 damping resistor to the switch filter a 74HC4051, do not substitute this chip as it is better than the ordinary 4051. An additional 1M0 resistor could be switched in parallel to the damping resistor for faster response.

The MAX494 amp "B" is just a buffer with a high impedance input. It is followed by a LowPass filter "C" to restore a nice sine wave. Amp "D" is a comparator used to generate a square wave of the signal, the comparison point is the middle voltage of the signal generated by the 62k~ resistor and the .47 uF cap at pin 13 of amp "D".

The whole analogue circuit operation is centred around 2.5 volts generated by the voltage divider of the two 2.2k~ resistors, 47 uF and .1uF caps.

A DC voltage proportional to the peak of the filtered input signal is generated by a 1N4148 diode and associated filters, this signal is called SIGLVL. This signal is maximum when there is no modulation.

The PIC16C72 inputs two analogue signals, a calibration voltage at pin 2 (install a second 10k pot and a SPDT switch to provide the doppler with the calibration for two radios), and the input signal level at pin 3. It also generates the capacitors filter switching signals pins 4, 5 and 6, the antennas switching signals at pins 11, 12, 13 and 14, the + commons for the display at pins 15, 16, 17 and 18 and the 0 volt to the cathodes of the LEDs at pins 21 to 28.

3- SOFTWARE DESCRIPTION

The software first check the CAL pot to set the proper direction, then measure the amplitude of the input signal to set flags signalling overload and squelched conditions.

Prescaler and counter TMR0 generate an interrupt at a rate of 16 kHz. 500 turn per second times 32 counts = 16000 Hz.

The interrupt loop switches the signals to the 500 Hz digital filter, changes the antennas, detect the phase of the incoming signal, averages the last 2 returns, set in the calibration, activates the display and advances the 32 count counter.

4- ANTENNAS

The switching signals are from +5 volt to 0 volt. Request modified software for opposite signals.

It will drive directly the Jim Sorenson KA4IIA switcher with MAR-4 preamps. I changed the coupling capacitors to a value of 100 pF, 2 of them are used in parallel at each coupling point. I also changed the chokes to 5 turns around 2 ferrite beads for VHF-UHF use.

It will also drive Joe Moell K0OV new wide band switcher, do not forget that the ground plane must be at +3.7 volt instead of 0 volt.

And It will drive the original ROANOKE antenna switcher with 680R resistors added in series with the switching lines.

5- CONSTRUCTION HINTS AND SUGGESTIONS

To eliminate Microprocessor noise, mount the doppler in a metal box.

Make the 180 degree light a different color to indicate signal overload.

On the display board, with insulated jumper wire, connect the 4 "D1" points together with the "D1" input wire. Do the same with "D2", "D3" etc.

Use a One Time Programming 20mHz PIC device for reduced cost. (no upgrade then possible)


On the WEB, ask for free samples from MAXIM for the MAX devices.

Use the brightest possible diffused red LEDs for maximum visibility and viewing angle.

Please put my call Letters on the front panel, its my only reward.

GOOD LUCK, Let me know how you are doing and if you like its performance by sending me a QSL card with your comments.

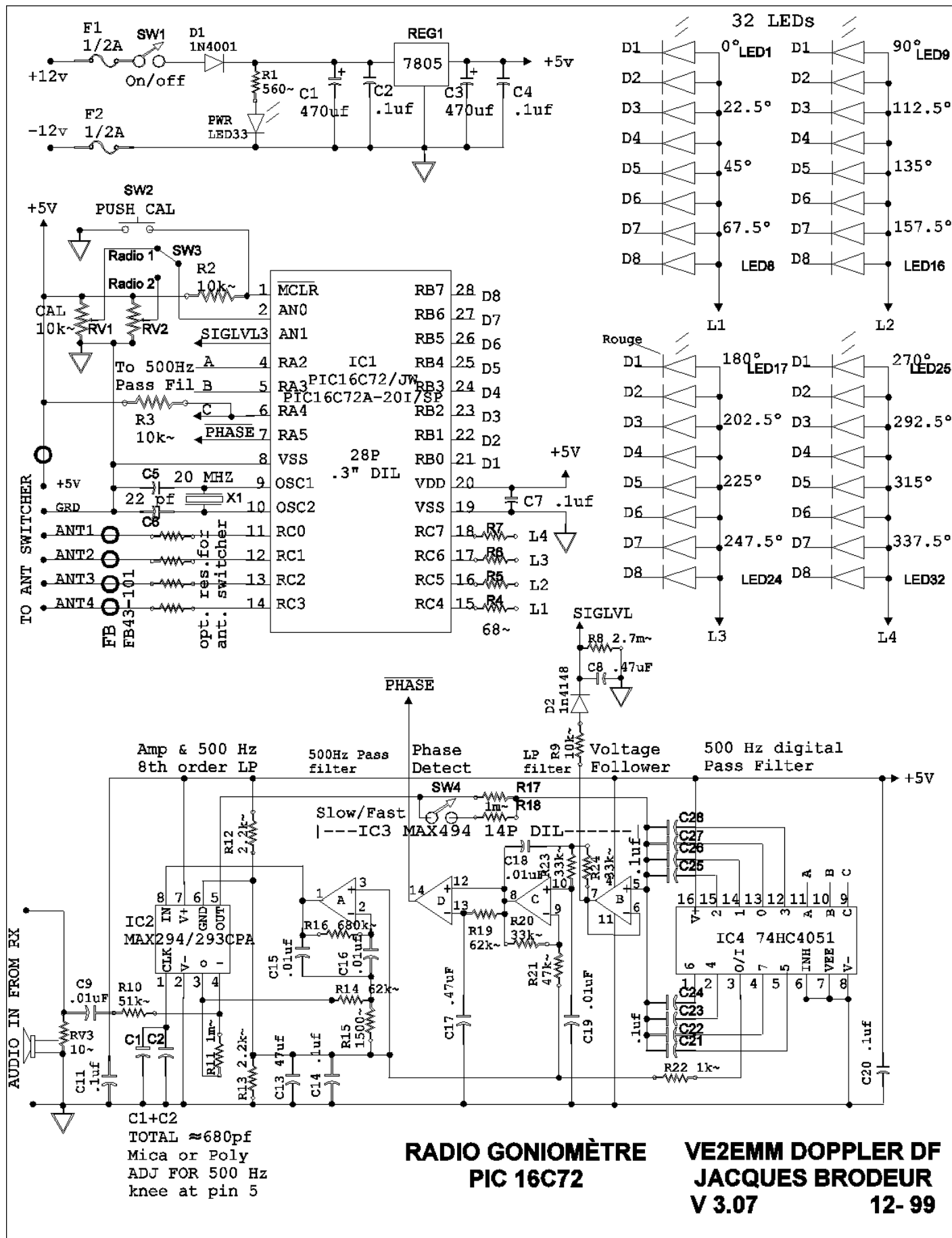Jacques Brodeur VE2EMM
5034 Joseph-A-Rodier
Montreal, Qc
Canada H1K 5E1



Sections alimentation & numerique - Power & digital sections

C1,3 = 470 uF 25 V electrolytic axial leads
C2,4,7 = .1 uF ceramic
C5,6 = 22 pF ceramic
D1 = Any rectifier diode ex.: 1N4001 - 1N4007
F1,2 = 3AG 1/2 Amp fuse
IC1 = Windowed PIC16C72/JW DIGI-KEY
or PIC16C72-20I/SP No upgrade then possible DIGI-KEY
LED 1 = Green diffused high brightness LED
LED 2-16, LED 18-32 = Red diffused high brightness LED
LED 17 = Green diffused high brightness LED
LED 33 = Red or green diffused high brightness LED
R1 = 560 Ohms 1/4 Watt
R2,3 = 10 kOhms 1/4 Watt
R4,5,6,7 = 68 Ohms 1/4 Watt
REG1 = 7805 5 V regulator TO-220 DIGI-KEY
RV1,2 = 10 kOhms 1/4 Watt variable DK pn. D4AA14-ND
SW1 = Miniature toggle SPST
SW2 = N.O. miniature push button
SW3 = Miniature toggle SPDT
X1 = 20MHz microprocessor Xtal DIGI-KEY

Section traitement audio - Audio processing section

C8 = .47 uF ceramic
C9,15,16,18,19 = .01 uF ceramic
C11,14,20,21,22,23,24,25,26,27,28, = .1 uF ceramic
C12 = TOTAL of 2 capacitors = 680 pF MICA OR POLY. trimm for 500 Hz
C13 = 47 uF electrolytic 10 V axial leads
C17 = .47uF ceramic
D2 = 1N4148
IC2 = MAX294CPA Low pass filter MAXIM free sample or Web purchase
IC3 = MAX494CPD quad rail to rail OP amp DIGI-KEY or MAXIM
IC4 = 74HC4051 do not substitute
R8 = 2.7 mOhms 1/4 Watt
R9 = 10 kOhms 1/4 Watt
R10 = 51 kOhms 1/4 Watt
R11,17,18 = 1 mOhms 1/4 Watt
R12,13 = 2.2 kOhms 1/4 Watt
R14,19 = 62 kOhms 1/4 Watt
R15 = 1.5 kOhms 1/4 Watt
R16 = 680 kOhms 1/4 Watt
R20,23,24 = 33 kOhms 1/4 Watt
R21 = 47 kOhms 1/4 watt
R22 = 1 kOhms 1/4 Watt
RV3 = 10 Ohms 1 Watt variable or 10 Ohms fixed resistor
SW4 = Miniature toggle SPST

Divers : - Misc. :

Box, connectors, wire, PC boards etc...

January 19, 2000

Mr. Brodeur,

Digikey distributes only a small handful of our many products.

The MAX293/MAX294 should still be available through the free samples request page, and through "Maxim Distribution" as well. From Canada you can call:

Canada Maxim Distribution 888-MAXIM-IC


There is one technical issue with the current parts. There has been a redesign which should be tested this engineering quarter. The current parts have occasional internal oscillator problems. If you're using an external oscillator, the problem is not an issue. However, if using the internal oscillator, the oscillator may operate intermittently, stall, then restart, etc. There is a "waiver" form which states that operation with internal oscillator is not guaranteed.

Many customers use an external oscillator for more accurate corner frequencies, and those customers are unaffected by the problem.


Best Regards,

AppsTechsupport
Maxim Applications Engineering
MH012000-104


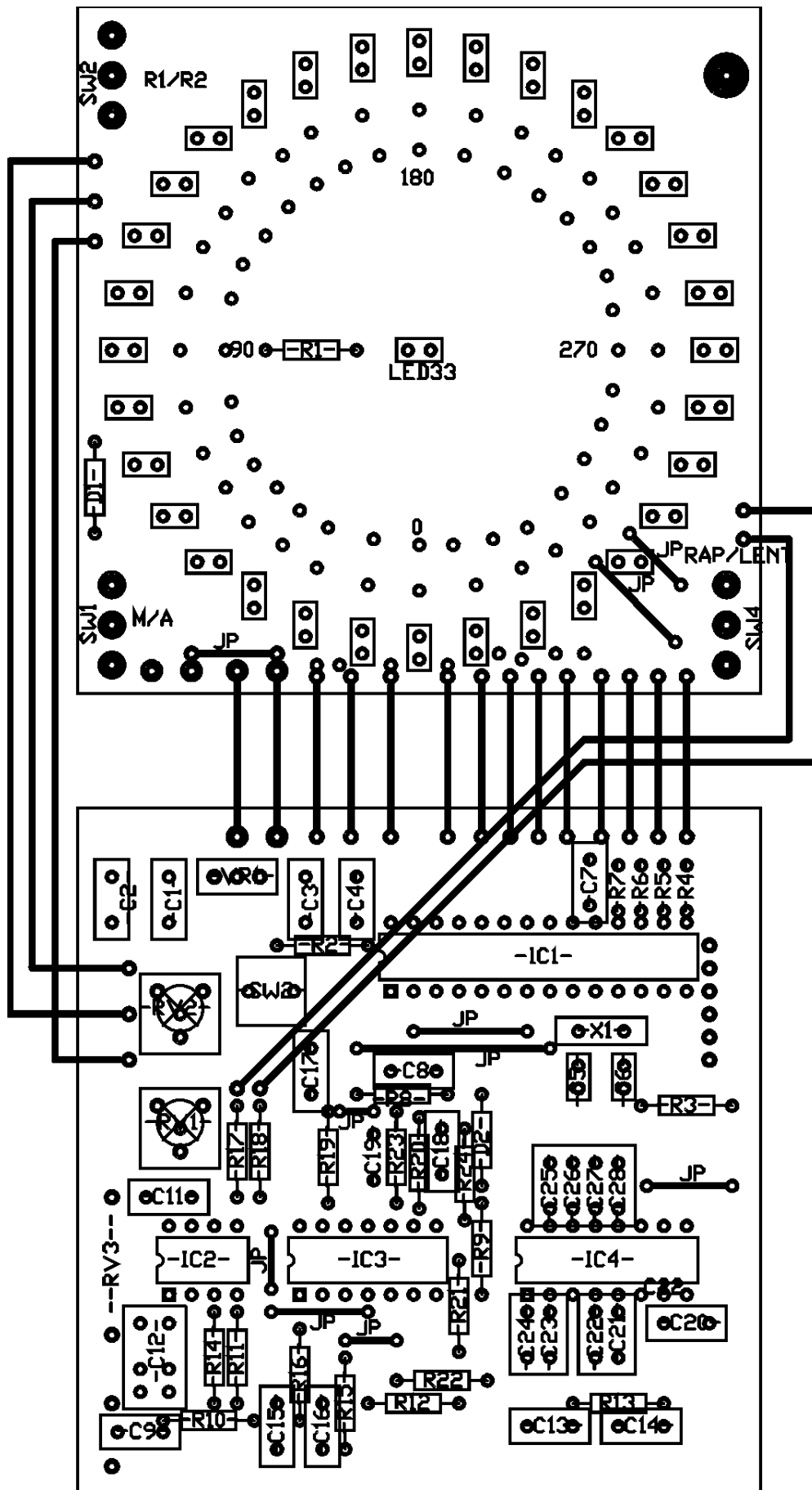
p.s. other dist.
US/Canada Distributors
Name Phone
Maxim Distribution 888-MAXIM-IC
Arrow Electronics 800-777-2776
CAM RPC 412-963-6202
Digi-Key Corp. 800-344-4539
Elmo Semiconductor 818-768-7400
Avnet Electronics Marketing 800-332-8638
Nu Horizons 516-396-5000



Component Location

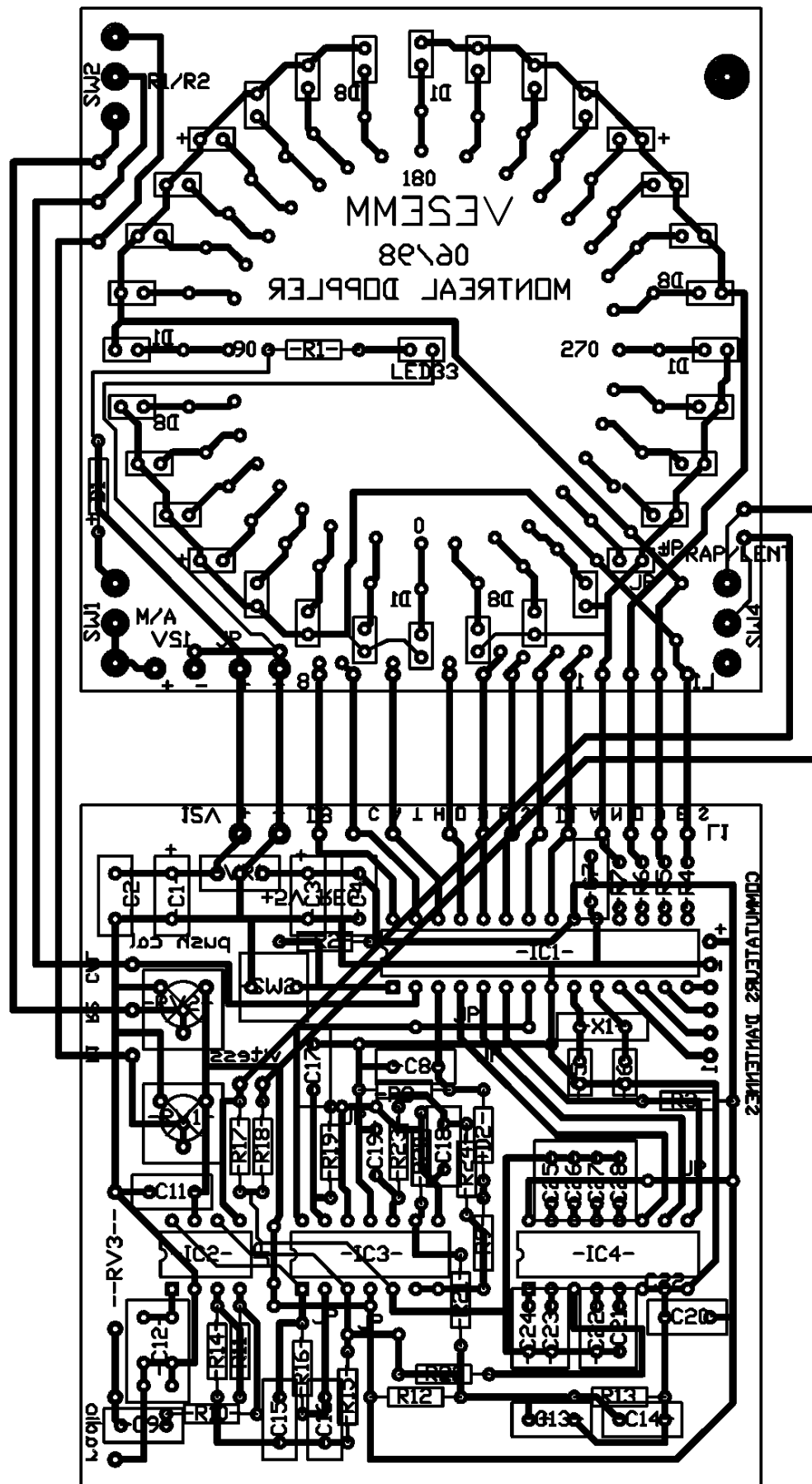

Components Location and PCB

  

3"

3 1/16"

User Comments and Suggestions:

From Ian, G8PWE:

Thu, 02 Sep 1999 00:07:08 +0100

From:

Ian Ashford <ian.ashford@dtm.ntl.com>

Cher Jacques,

Today I tested your design of DF unit .

I was very Impressed with the performance ESPECIALLY the averaging work of the PIC controller.

I have sent you some photos of my build for you to publish if you want.

Notes:

- 1)The unit is built in double sided PCB (painted green)
- 2)I had to decouple PIC noise from antenna array switching wires with 47uh series choke.
- 3)Antenna array is Roanoke wideband with switchbox magnetic mount on roof -very pleased with its performance compared with earlier designs.
- 4)Roanoke antenna - the 5v-3v dropper is a green LED in the switchbox which checks DC operation of system.
- 5) I will put your callsign on the top panel now work is finished.
- 6)Next stage is to interface to APRS using N7ILUE unit.

a bientot

Ian G8PWE

From Mike, K5ATM:

Hello all

I just completed the construction of my Montreal Doppler / wide band antenna array and thought I would pass on my comments and suggestions. In particular I had a great deal of trouble with calibration stability.

See below for details. You will also see in the pictures I have not labeled the unit yet. I am still waiting for my white dry transfer letters to arrive.

Construction

I ordered the 3 board plus PIC chip set from Far Circuits. This set includes a display board, a controller board and a wide range antenna switcher board (see Joe Moell's web site (<http://members.aol.com/homingin/newdopant.html>). This made construction very straight forward. The only surprises were:

- Some holes on the PC boards were not drilled
- The controller board is not designed to supply the 3.7 volt "ground" needed by the wide range antenna switcher. I used an LED / resistor combo to generate the required "ground".
- The display board needs a large number of jumpers. I used wire-wrap techniques for this step.

Here is a picture of the inside of my unit. The box is from Radio Shack (270-274, \$12.99). Note the amp attached to upper corner of the speaker. This provides the ability to control the amplitude of the audio without effecting the signal level presented to the Doppler electronics. The amp was obtained from Radio Shack in kit form (RSU 12126918, \$12.99) and can produce up to 7W of power. The metal frame of the speaker serves as a heat sink for the amp chip.

Here is a picture of the outside of my unit. The controls along the bottom (from left to right) are:

Power

Audio volume

Fast/Slow

Radio 1 / Radio 2

Audio select (see below)

The VU meter is connected to the output of the synchronous detector (pin 7 of IC3) through a 10uF capacitor. This provides a way to monitor the signal level that is presented to the PIC chip. The 10uF capacitor gives just enough coupling to cause the overload LED to flash just as the needle enters the red area of the meter.

The LED above the VU meter is the LED used to generate the 3.7 volt "ground".

The "audio select " switch selects what signal is sent to the 7 watt audio amp. In one position the audio from the radio is selected. This gives the user the ability to monitor the raw signal from the radio. In the other position, the output from the synchronous detector is sent to the amplifier. This gives the user the ability to monitor the pure 500Hz Doppler tone.

Friction of the LEDs against the holes drilled in box is all that holds the display board / electronics board in place.

Here is a drawing of the modifications I made to the base design.

Antenna

I did not use a solid piece of copper for the base of the antenna array. I placed a 4" by 4" piece of copper in each corner of the wooden base and connected copper clad steel welding rods to the pads. This was much cheaper and seems to give good results.

I wound my own coils for the antenna switcher board. Each coil consisted of 24 turns of #26 magnet wire on a 3/16 inch drill. I did not have any Q-dope so I used clear finger nail polish to hold the coils together.

MPN-3401 PIN diodes are much easier to work with than EGC555. The EGC part is a "through-hole" part but is very close to a surface mount device in terms of size. Get the 3401s if you can.

Testing

I used an MFJ antenna analyzer to test the antenna array. I suspect any SWR meter with a QRP transmitter would work. I stress low power though. Don't blow up your PIN diodes!!! I connected 3.7v to the "ground" terminal on the switched board and grounded (0 volts) the antenna 1 select lead (the wire that would normally go to IC1 pin 11). This forward biased the diodes associated with antenna 1. I then connected the antenna analyzer to the cable that would normally go to the receiver and verified the antenna was "turned on" and trimmed the welding rod to a good SWR. I repeated for antennas 2-4. I ended up with an SWR of 1.3 at 146 Mhz on all 4 antennas.

After verifying the PIC chip was running (by looking at the antenna select lines with a scope) I used the PIC chip / antenna array to generate a test signal that would allow me to debug the analog electronics on the bench. I connected the "bottom" of a 20K pot to ground (not the floating ground) and the wiper to audio in. I then connected the "top" of the pot to the copper clad welding rod used to make antenna 1 and adjusted the pot to give a good signal (one non flashing LED on the display board). I then moved the "top" of the pot to antenna 2, then antenna 3 and then antenna 4. Each time, the direction indicated on the display board would jump 90 degrees. This signal was also used to adjust the 500Hz low pass filter by watching the waveform on pin 5 of IC2 while adjusting capacitors attached to pin 1 of IC2.

A problem with calibration

I installed the unit in my truck and set off to gain some experience using a Doppler DF unit. Calibration went as expected and the unit seemed to work as advertised. Later I noticed the unit continued to work but the calibration seemed to have shifted by 90 degrees or so. I figured I simply made a mistake in the initial calibration and recalibrated. Again the unit worked for a while but then the calibration slipped. A while later is slipped back.

To make a long story short, I spent several weeks trying to find out what was wrong. The unit would work for days at a time on the bench without so much as a hiccup but would fail to keep calibration in the truck. The problem seemed to be environmental and I suspected vibration in the antenna array or dirty power.

I finally tracked the problem down to temperature sensitive capacitors. Specifically C9, C15, C16, C18, and C19. These are all .01uF capacitors used to filter the audio signal. My original capacitors were Digikey P4300A-ND. These capacitors seem to be EXTREMELY sensitive to temperature changes. I eventually found that calibration would change by over 180 degrees between a cold car in the morning and a car that had become hot inside after being parked outside for a few hours! Replacing these capacitors with high quality units fixed the problem.

It really was necessary to replace all 5 capacitors. Once I understood what was going on I could use a hair dryer to to make the unit fail. I replaced the capacitors one at a time--testing after each replacement. Each

time performance improved but did not become solid until all 5 were replaced.

How does it work

The unit works great! Most of my experience so far is with local repeaters. The display is solid (+/- 1 one light) as I drive around town. Not much experience on weak signals yet.

I find it is important to keep moving to get accurate bearings.

What would I do different?

The physical layout of the boards makes mounting difficult. There is just no place to drill mounting holes except near the 225 degree light. I think if I was to start over I would connect the two boards together with a set of .01 inch headers. The combination of the header/pin set at one end and a bolt / spacer combo at the other would make for a tightly coupled unit.

The LEDs I used for the dial were clear high brightness units. In retrospect this was probably a mistake. I was worried bright sunlight might make viewing the LEDs difficult. On axis these LEDs are very bright. At night they are too bright. Off axis the defused LED used for the "floating ground" is much easier to see than the dial LEDs. This is important if you have a co-pilot who must also see the display.

I also think I will eventually scrap the antenna and go to the mag mount antenna array described on Joe Moell's page. It just seems cleaner. Maybe I will mount the current antenna array to the roof of my house and make a base direction finder.

Would I do it again?

You bet! Thank you very much Jacques Brodeur. A great project!!!!

Parts List

Here is a parts list I generated. Please, if you use this list only consider this as a start. Double check all part numbers. Prices were from the catalog in effect in February 2000.

K5ATM, mycall@rt66.com

Label	Description	Quantity	Source	Part Number	Price	Total	Comments
C1,3	470 uF 25 V electrolytic axial leads (I think radial)	2	Digikey	P5155-ND	0.44	0.88	
C2, 4, 7, 11, 14, 20, 21, 22, 23, 24, 25, 26, 27, 28	.1 uF ceramic	20	Digikey	P4201-ND	0.23	4.60	(must order in lots of 10)
C5,6	22 pF ceramic	10	Digikey	P4016A-ND	0.10	1.00	(must order in lots of 10)
C8, 17	.47uF ceramic	2	Digikey	P4967-ND	0.72	1.44	
C9, 15, 16, 18, 19	.01 uF ceramic		See note under testing above				
C10 -- unused							
C12a	120pF	1	Digikey	P3121-ND	0.24	0.24	Combine to total 680pF
C12b	100pf	1	Digikey	P3101-ND	0.24	0.24	Combine to total 680pF
C12c	150pF	1	Digikey	P3151-ND	0.24	0.24	Combine to total 680pF
C12d	560pF	1	Digikey	P3561-ND	0.24	0.24	Combine to total 680pF
C12e	4.5-65 pF trimmer	1	Digikey	SG3009-ND	1.68	1.68	Combine to total 680pF
C13	47 uF electrolytic 10 V radial leads	1	Digikey	P5137-ND	0.17	0.17	

D1 (+ two diodes for the 3.7v "ground"	Diode,1N4001, 1N4007, etc.	1	Digikey	1N4001MSCT-ND	0.43	0.43	cut tape -- 10 units
D2	Diode, 1N4148	1	Digikey	1N4148MSCT-ND	0.53	0.53	cut tape -- 10 units
F1,2	3AG 1/2 Amp fuse	1	Digikey	F112-ND	1.95	1.95	(package of 5)
Fuse Holder	2 position fuseholder board	1	Digikey	3537K-ND	1.57	1.57	
IC1	PIC16C72-20/SP É OR	0	Digikey	PIC16C72-20/SP-ND	7.35	0.00	This chip comes with the Far Ckt 3 board set
IC1	PIC16C72/JW	0	Digikey	PIC16C72/JW-ND	14.03	0.00	Use this if you want to change pgm
IC2	MAX293CPA (MAX294CPA) Low pass filter	0	Maxim	MAX293CPA	5.92	0.00	Try getting a free one!
IC3	MAX494CPD quad rail to rail OP amp	0	Maxim	MAX494CPD	6.42	0.00	Try getting a free one!
IC4	74HC4051 8-channel analog mux	1	Digikey	MM74HC4051N-ND	0.66	0.66	
Socket-1	28 pin IC socket	2	Digikey	AE9814-ND	0.57	1.14	Need 2. Digikey 28 pin sockets are .6 inches wide

Socket-2	8 pin IC socket	1	Digikey	AE9808-ND	0.36	0.36	
Socket-3	14 pin IC socket	1	Digikey	AE9814-ND	0.57	0.57	
Socket-4	16 pin IC socket	1	Digikey	AE9816-ND	0.65	0.65	
REG1	7805 (LM340) 5 V regulator TO-220	1	Digikey	LM340T-5.0-ND	0.70	0.70	
LED 1, 33	Green high brithness LED (40 mcd) See "What would I do different" above	2	Digikey	160-1131-ND	0.23	0.46	0 deg and power. I used high brightness clear LED for max daytime visibility
LED 2-16, LED 18-32	Red high brithness LED (40 mcd)	3	Digikey	160-1128-ND	1.75	5.25	misc deg. Light (3 pkg of 10)
LED 17	Yellow high brithness LED (40 mcd)	1	Digikey	160-1134-ND	0.23	0.23	180 deg. Light
R1	560 Ohms 1/4 Watt	1	Digikey	560QBK-ND	0.28	0.28	(package of 5)
R2,3,9	10 kOhms 1/4 Watt	1	Digikey	10KQBK-ND	0.28	0.28	(package of 5)
R4,5,6,7	68 Ohms 1/4 Watt	1	Digikey	68QBK-ND	0.28	0.28	(package of 5)
R8	2.7 mOhms 1/4 Watt	1	Digikey	2.7MQBK-ND	0.28	0.28	(package of 5)

R10	51 kOhms 1/4 Watt	1	Digikey	51KQBK-ND	0.28	0.28	(package of 5)
R11,17,18	1 mOhms 1/4 Watt	1	Digikey	1.0MQBK-ND	0.28	0.28	(package of 5)
R12,13	2.2 kOhms 1/4 Watt	1	Digikey	2.2KQBK-ND	0.28	0.28	(package of 5)
R14,19	62 kOhms 1/4 Watt	1	Digikey	62KQBK-ND	0.28	0.28	(package of 5)
R15	1.5 kOhms 1/4 Watt	1	Digikey	1.5KQBK-ND	0.28	0.28	(package of 5)
R16	680 kOhms 1/4 Watt	1	Digikey	680KQBK-ND	0.28	0.28	(package of 5)
R20,23,24	33 kOhms 1/4 Watt	1	Digikey	33KQBK-ND	0.28	0.28	(package of 5)
R21	47 kOhms 1/4 watt	1	Digikey	47KQBK-ND	0.28	0.28	(package of 5)
R22	1 kOhms 1/4 Watt	1	Digikey	1.0KQBK-ND	0.28	0.28	(package of 5)
RV1,2	10 k 1/4 Watt variable	2	Digikey	D4AA14-ND	0.33	0.66	
RV3	10 Ohms 5 Watt variable	1	Digikey	CT2151-ND	3.20	3.20	
SW1, SW3, SW4	Miniature toggle SPDT	0	Digikey	CKN1021-ND	3.75	0.00	On/Off, Radio 1/2, Fast/Slow. I did not order. I had these

SW2	N.O. miniature push button	1	Digikey	P8070SCT-ND	0.30	0.30	Push to calabrate switch
FB1-5	Ferrite beads (Miller FB43-101)	5	Digikey	M2304-ND	0.12	0.60	No FB43-101 in Miller cat. Used FB43110
X1	20mHz uProcessor Xtal	1	Digikey	CTX062-ND	0.94	0.94	
C101-109	680 pF poly (for switcher)	9	Digikey	P3681-ND	0.24	2.16	
L101-104	1.5 uH coil (for switcher)						Hand wind, air core, 24 turns of #26 wire on 3/16" form. Radio Shack has wire.
R101-104	220 Ohm 1/4 Watt (base of antennas)	1	Digikey	220QBK-ND	0.28	0.28	(package of 5) Also use 1 in the 3.7V ckt--or order a 330 Ohm
D101-108	MPN-3401 PIN diodes (switcher and base of antennas)	8	www.debco.com	MPN-3404	1.00	8.00	\$1 each + \$5 min shippingso buy extra. I like these better than EGC555 (easer to mount)

PC board set + PIC	3 board set + PIC chip	1	Far Circuits		35.00	35.00	Check to see if all holes are drilled before starting!!!!
controller to antenna connector							I used a Radio Shack 6 pin DIN connector
Antenna feed line (from switcher to controller)	RG-58	X feet					I picked up at "junk" store
Antenna to switcher coax	RG-174	~80"					I pickes up at "junk" store
Antennas	1/4 wave antenna	4					I used 3/32 copper clad steel welding rod. All radials and antennas were about \$6.00
Antenna connectors	BNC connectors (Male)	4					I used the method in Joe Moell's book. \$ used connectors were \$2.00
Radials	1/4 wave radial	8					See antenna note above
Radial connectors	Terminal lugs (from local hardware store) ~\$1.50						I used the method in Joe Moell's book.

Antenna ground plane	19" x 19" double sided PC board	1					
Antenna base	19" x 19" x 1/2" plywood	1					
Box							
				Total		~\$80.00	

key words for altavista, yahoo, etc:

Montreal Doppler, building a Montreal Doppler, testing the Montreal Doppler, calibration problems with the Montreal Doppler.

;== DOPPLER DF PAR JACQUES BRODEUR == VE2EMM ===== REV. 1

;Free use granted to HAM RADIO OPERATORS only for HAM RADIO purpose.

;Please mention VE2EMM when using it. It is my only reward.

;No resale permitted.

DOPPLER DF, CONTROLE PAR PIC16C72

Liste des entrees/sorties du microcontrôleur

8 sorties lampes affichage	B0-B7	
4 communs lampes affichage		C4-C7
4 sorties antennes	C0-C3	
1 Entree analogue CAL		A0 ;Direction des lampes
1 Entree analogue SIGLVL		A1 ;Niveau du signal
3 Sorties filtre digital ROANOKE		A2-A4
1 entree signal de phase PHASE/		A5

```
LIST      P=16C72
RADIX     HEX
INCLUDE   P16C72.INC
__CONFIG _HS_OSC&_PWRTE_ON&_CP_OFF&_WDT_ON&_BODEN_ON
```

ALLOCATION DES MEMOIRES, VALEURS ET BITS

```
CBLOCK    0X20
STA_W          ;STACK POUR LE W
STA_STATU      ;STACK POUR LE STATUS
ROSE           ;COMPTEUR DE DEGRES
DIR_1          ;DIRECTION MOYENNE DE LA PHASE
DIR_2          ;DIRECTION DE LA PHASE
ECAR
DIRECTION      ;POUR AFFICHER
MEMTMP1        ;Memoire temporaire tout usage
MEMTMP2
DRAPEAU        ;Flags
               ;b0=lecture de la direction deja faite
               ;b1=SIGLVL overload
               ;b2=Demander une conversion de SIGLVL
               ;b3=SIGLVL recepteur silencieux
PHASAGE        ;Deplacement de la direction (CAL)
SIGLVL         ;Niveau du signal au filtre
TIMR1          ;pour le clignoteur 180 degre
TIMR2          ;Pour le clignoteur squelch
BIT            ;Memoire pour la bit a clignoter
ENDC
```

---DEBUT DU PROGRAMME-----

```
ORG      0X000
GOTO     INIT
```

===== INTERRUPTION =====

```
ORG      0X004
MOVWF    STA_W      ;PUSH le reg W
SWAPF    STATUS,W   ;PUSH le reg STATUS
MOVWF    STA_STATU
```

```

        MOVLW    D'178'      ;178 pour 20 mHz pour 500Hz
        MOVWF    TMR0        ;RESET TMR0
;
;
;--CHANGER D'ANTENNE-----
;
        MOVF     ROSE,W      ;CHANGER LES CONDENSATEURS DU FILTRE DIGITAL
        MOVWF    PORTA       ;bits 2,3,4

ANT1     MOVLW    D'0'        ;ANTENNE 1
        XORWF    ROSE,W      ;TESTER POUR 0 degree
        BNZ      ANT2
        BCF      PORTC,0     ;Activer L'antenne 1
        NOP
        BSF      PORTC,3     ;Deconnecter l'antenne 4

ANT2     MOVLW    D'8'        ;ANTENNE 2
        XORWF    ROSE,W      ;TESTER POUR 90 degrees
        BNZ      ANT3
        BCF      PORTC,1     ;Activer L'antenne 2
        NOP
        BSF      PORTC,0     ;Deconnecter l'antenne 1

ANT3     MOVLW    D'16'       ;ANTENNE 3
        XORWF    ROSE,W      ;TESTER POUR 180 degrees
        BNZ      ANT4
        BCF      PORTC,2     ;Activer L'antenne 3
        NOP
        BSF      PORTC,1     ;Deconnecter l'antenne 2

ANT4     MOVLW    D'24'       ;ANTENNE 4
        XORWF    ROSE,W      ;TESTER POUR 270 degrees
        BNZ      TESTER
        BCF      PORTC,3     ;Activer L'antenne 4
        NOP
        BSF      PORTC,2     ;Deconnecter l'antenne 3
;
;
;--TESTER LE SIGNAL-----
;
TESTER    BTFSS    DRAPEAU,3 ;Si SIGLVL < SQUELCH clignoter lentement
                        ;l'affichage
        GOTO     AFF_OVERL    ;SIGLVL au dessus du SQUELCH
        BTFSS    TIMR2,0     ;SIGLVL sous le SQUELCH * * * * *
        GOTO     AFFICHER    ;Allumer la lampe
        MOVLW    0XFF        ;Eteindre la lampe *
        MOVWF    PORTB
        GOTO     AVANCER     ; * * * * *

AFF_OVERL    BTFSS    DRAPEAU,1 ;Tester pour OVERLOAD du niveau de signal
        GOTO     PHASE        ;Afficher la direction * * * *
        BTFSS    TIMR1,6     ;Clignote rapidement la lampe OVERLOAD, 180 deg.
        GOTO     CLI_ON
        MOVLW    D'32'       ;Lampe eteinte
        MOVWF    DIRECTION
        GOTO     AFFICHER    ;Afficher la direction
CLI_ON     MOVLW    D'16'     ;Lampe allumee
        MOVWF    DIRECTION
        GOTO     AFFICHER    ;Continuer * * * * *
;
;
;--LIRE LA PHASE-----
;
PHASE     BTFSS    PORTA,5    ;Tester pour 1 changement par revolution
        GOTO     LIREPHASE   ;Lire la PHASE
        BTFSS    LIREPHASE   ;0=lire

```



```

        BCF      DRAPEAU,0 ;1=ne pas lire
        GOTO     AVANCER
LIREPHASE BTFSF   DRAPEAU,0 ;Deja lu si 1, Lire si 0
        GOTO     AVANCER ;Terminer direction est deja lu
        MOVF     ROSE,W    ;Ramasser la direction de ce cycle
        MOVWF    DIR_2     ;DIR_2=Direction presente -- DIR_1=Direction precedente
        BSF      DRAPEAU,0 ;Indique que la lecture est faite, bit a 1
;
;--CALCULER LA MOYENNE DE 2 RETOURS-
        MOVF     DIR_2,W    ;Dir_2 doit etre plus grand que DIR_1
        SUBWF    DIR_1,W
        BTFSS    STATUS,C
        GOTO     CALCUL    ;Si DIR_1 plus petit que DIR_2

        MOVF     DIR_1,W    ;Echanger DIR_1 et DIR_2
        MOVWF    MEMTMP1
        MOVF     DIR_2,W
        MOVWF    DIR_1
        MOVF     MEMTMP1,W
        MOVWF    DIR_2

CALCUL   MOVF     DIR_1,W    ;ECAR = DIR_2 - DIR_1
        SUBWF    DIR_2,W
        MOVWF    ECAR
        CLRC     ;DIR_1 = (ECAR / 2) + DIR_1
        RRF      ECAR,W
        ADDWF    DIR_1,F

        MOVLW    D'16'     ;IF ECAR <16 THEN LECT_FAITE ELSE
        SUBWF    ECAR,W
        BNC      CAL

SUITE    MOVLW    D'16'     ;Si DIR_1 < 16
        SUBWF    DIR_1,W
        BNC      ADD16

        MOVLW    D'16'     ;IF NOT DIR_1 = DIR_1 - 16
        SUBWF    DIR_1,F
        GOTO     CAL

ADD16    MOVLW    D'16'     ;IF DIR_1 < 16 THEN DIR_1 = DIR_1 + 16
        ADDWF    DIR_1,F
;
;--CALIBRER-----
;
CAL       MOVF     PHASAGE,W ;Ajouter la calibration
        ADDWF    DIR_1,W
        MOVWF    DIRECTION
        MOVLW    D'32'
        SUBWF    DIRECTION,W ;
        BC       SOUSTRAIRE ;Si 32 et plus soustraire
        GOTO     AFFICHER
SOUSTRAIRE MOVLW    D'224'   ;Soustraire 32
        ADDWF    DIRECTION,F
;
;--AFFICHAGE-----
;
AFFICHER MOVLW    0X02      ;Aller a la page 0x200
        MOVWF    PCLATH
        CLRC     ;Afficher les lampes de direction
        RLF      DIRECTION,W
        CALL     LAMPES
        MOVWF    PORTB     ;*****Cathode des lampes

```

```

        RLF          DIRECTION,W          ;Chercher les anodes
        ADDLW        0X01
        CALL         LAMPES
        MOVWF        MEMTMP1 ;*****Sauver les anodes des lampes
        CLRF         PCLATH
        MOVF         PORTC,W
        ANDLW        B'00001111' ;Charger les antennes
        IORWF        MEMTMP1,W           ;Ajouter les lampes
        MOVWF        PORTC ;*****Mise a jour du port C
;
;
;--AVANCER LE COMPTEUR-----
;
;
AVANCER  INCF        ROSE,F          ;AVANCER LE COMPTEUR
        MOVLW        D'32'
        SUBWF        ROSE,W          ;TESTER SI COMPTE MAXIMUM
        BNC          POP             ;ARRETER LE COMPTEUR A 31
        CLRF         ROSE            ;Commencer a 0
        BSF          DRAPEAU,2 ;Commander une conversion du SIGLVL
        INCF         TIMR1,F
        SKPNZ
        INCF         TIMR2,F
;
;
;--TERMINER-----
;
;
POP      BCF          INTCON,T0IF ;Rappeler IE FLAG T0IF de L'OVERFLOW
        ;DE TMR0
        SWAPF        STA_STATU,W      ;Restorer le reg STATUS
        MOVWF        STATUS
        SWAPF        STA_W,F          ;Restorer le reg W
        SWAPF        STA_W,W
        RETFIE
;
;
=====
;--- INITIALISATION ET LECTURE DE LA CALIBRATION -----
;
;
INIT     CLRF        PORTA
        CLRF        PORTB
        CLRF        PORTC
        ;Charger la calibration de l'affichage
        BSF          STATUS,RP0      ;Page 1
        MOVLW        B'00000100'
        MOVWF        ADCON1 ;Analogue AN0 AN1 AN3
        BCF          STATUS,RP0      ;Page 0
        MOVLW        B'11000001' ;Clock RC, convertir AN0
        MOVWF        ADCON0 ;
        MOVLW        D'60'
        MOVWF        MEMTMP1
WAIT     DECFSZ      MEMTMP1,F
        GOTO         WAIT ;Stabiliser l'entree
        BSF          ADCON0,GO        ;Demarrer le convertisseur A/N
ANCONVER BTFSF      ADCON0,GO        ;Si 0, terminee
        GOTO         ANCONVER ;Attendre la fin de conversion
        MOVF         ADRES,W ;
        MOVWF        PHASAGE ;Sauver la calibration
        CLRC
        RRF          PHASAGE,F ;127 max
        CLRC
        RRF          PHASAGE,F ;67 max
        CLRC
        RRF          PHASAGE,F ;31 compte max
;
;
;---Operation normale-----
;
;

```

```

        CLRF      ADCON0
        BSF       STATUS,RP0          ;Page 1
;
        MOVLW    B'00000110' ;RA TOUT DIGITAL
;
        MOVWF    ADCON1
        MOVLW    B'00100011' ;0-1,5 entrees 2-4 sorties PORTA
        MOVWF    TRISA
        MOVLW    B'00000000' ;Tout en sortie PORTB
        MOVWF    TRISB
        MOVLW    B'00000000' ;Tout en sortie PORTC
        MOVWF    TRISC
        MOVLW    B'11010001' ;OPTION TOCS=internal CLK, PRE=/2, PSA=TMR0
        MOVWF    OPTION_REG
        MOVLW    B'10100000' ;INTCON GIE T0IE
        MOVWF    INTCON
        BCF      STATUS,RP0          ;Page 0

        MOVLW    D'00'      ;Conditions de depart des memoires
        MOVWF    ROSE
        MOVWF    DIR_1
        MOVWF    DIR_2
        MOVWF    DIRECTION
        MOVLW    0X0F      ;Deconnecter les antennes
        MOVWF    PORTC
        MOVLW    B'00000001'
        MOVWF    DRAPEAU
        MOVLW    D'178'
        MOVWF    TMR0
;
;---BOUCLE PRINCIPALE-----
;
PRINC      CLRWDT
          BTFSS    DRAPEAU,2 ;Temps de faire une conversion?
          GOTO     PRINC      ;Non
          BCF      DRAPEAU,2 ;Oui
          MOVLW    B'11001001' ;Clock RC, convertir AN1
          MOVWF    ADCON0
          MOVLW    D'60'
          MOVWF    MEMTMP2
WAIT1      DECFSZ   MEMTMP2,F
          GOTO     WAIT1      ;Stabiliser l'entree
          BSF      ADCON0,GO   ;Demarrer le convertisseur A/N
ANCONVER1  BTFSC    ADCON0,GO   ;Si 0, terminee
          GOTO     ANCONVER1   ;Attendre la fin de conversion
          MOVF     ADRES,W
          MOVWF    SIGLVL      ;0 a 256 = 0 a 5 volts
          MOVLW    D'115'      ;Test de bas niveau 2.2 VOLTS
          SUBWF    SIGLVL,W
          BNC      SQUELCH      ;Signal faible
          BCF      DRAPEAU,3 ;Signal plus grand que le minimum
          GOTO     TESTOVERL
SQUELCH    BSF      DRAPEAU,3 ;Pour eteindre l'affichage
TESTOVERL  MOVLW    D'170'      ;(256/5V)*3.4V=174 (Niveau de crete)
          SUBWF    SIGLVL,W
          BNC      SIGBON      ;Enlever le flag
          BSF      DRAPEAU,1 ;Indication de OVERLOAD
          GOTO     PRINC      ;Attendre
SIGBON     BCF      DRAPEAU,1 ;Pas de OVERLOAD SIGLVL bon
          GOTO     PRINC
;
;---LAMPES-----
;
LAMPES     ORG      0X200
          ADDWF    PCL,F

```

RETLW	B'11111110'	;D1 0
RETLW	B'00010000'	;L1
RETLW	B'11111101'	;D2 1
RETLW	B'00010000'	;L1
RETLW	B'11111011'	;D3 2
RETLW	B'00010000'	;L1
RETLW	B'11110111'	;D4 3
RETLW	B'00010000'	;L1
RETLW	B'11101111'	;D5 4
RETLW	B'00010000'	;L1
RETLW	B'11011111'	;D6 5
RETLW	B'00010000'	;L1
RETLW	B'10111111'	;D7 6
RETLW	B'00010000'	;L1
RETLW	B'01111111'	;D8 7
RETLW	B'00010000'	;L1
RETLW	B'11111110'	;D1 8
RETLW	B'00100000'	;L2
RETLW	B'11111101'	;D2 9
RETLW	B'00100000'	;L2
RETLW	B'11111011'	;D3 10
RETLW	B'00100000'	;L2
RETLW	B'11110111'	;D4 11
RETLW	B'00100000'	;L2
RETLW	B'11101111'	;D5 12
RETLW	B'00100000'	;L2
RETLW	B'11011111'	;D6 13
RETLW	B'00100000'	;L2
RETLW	B'10111111'	;D7 14
RETLW	B'00100000'	;L2
RETLW	B'01111111'	;D8 15
RETLW	B'00100000'	;L2
RETLW	B'11111110'	;D1 16
RETLW	B'01000000'	;L3
RETLW	B'11111101'	;D2 17
RETLW	B'01000000'	;L3
RETLW	B'11111011'	;D3 18
RETLW	B'01000000'	;L3
RETLW	B'11110111'	;D4 19
RETLW	B'01000000'	;L3
RETLW	B'11101111'	;D5 20
RETLW	B'01000000'	;L3
RETLW	B'11011111'	;D6 21
RETLW	B'01000000'	;L3
RETLW	B'10111111'	;D7 22
RETLW	B'01000000'	;L3
RETLW	B'01111111'	;D8 23
RETLW	B'01000000'	;L3
RETLW	B'11111110'	;D1 24
RETLW	B'10000000'	;L4
RETLW	B'11111101'	;D2 25
RETLW	B'10000000'	;L4
RETLW	B'11111011'	;D3 26
RETLW	B'10000000'	;L4
RETLW	B'11110111'	;D4 27
RETLW	B'10000000'	;L4
RETLW	B'11101111'	;D5 28
RETLW	B'10000000'	;L4
RETLW	B'11011111'	;D6 29
RETLW	B'10000000'	;L4
RETLW	B'10111111'	;D7 30
RETLW	B'10000000'	;L4
RETLW	B'01111111'	;D8 31

```
RETLW    B'10000000' ;L4
RETLW    B'11111111' ; 32 Toutes les lampes eteintes
RETLW    B'00000000' ;
```

```
;
;
;
;
;
```

=====

END